

University of Bahrain
College of Information technology
Department of Computer Engineering

Test (2)

Student Name	
I.D. No.	
Section	

Course Title: Digital Logic
Course number: ITCE 202-250
Semester: 1
Academic Year: 2014/2015
Duration : 1 hour
Date: 9th December 2014

Read the following before you start:

1. Write with PEN

2. Write your name, ID and section number
3. Answer all questions.
4. Write your answers on the attached sheets only.


Question	Mark
1 (20 Mark)	
2 (18 Mark)	
3 (20 Marks)	
4 (18 Mark)	
5 (24 Mark)	
Total (100)	

Question [1]: (20 Mark)

Implement the following Boolean function:

$$f(A, B, C) = \Sigma m(0, 3, 4, 7)$$

Using a 3-to-8 line decoder and:

 **a.** an extra OR gate.**b.** an extra NAND gate.**c.** an extra AND gate.**d.** an extra NOR gate.

Question [2]: (18 Marks)

Implement the following function with a 4-to-1 Multiplexer and a minimum number of logic gates:

$$F(a,b,c,d) = \Sigma m(0,1,4,7,8,9,10,15,)$$


Question [3]: (20 Marks)

A ROM that stores the values of the following arithmetic function is to be designed:

$$F = 2(a+b) \text{ where } a \text{ and } b \text{ are 2-bit binary numbers.}$$

a- Give the size of the ROM



b- Draw the internal structure of the ROM showing the last 3 memory lines.

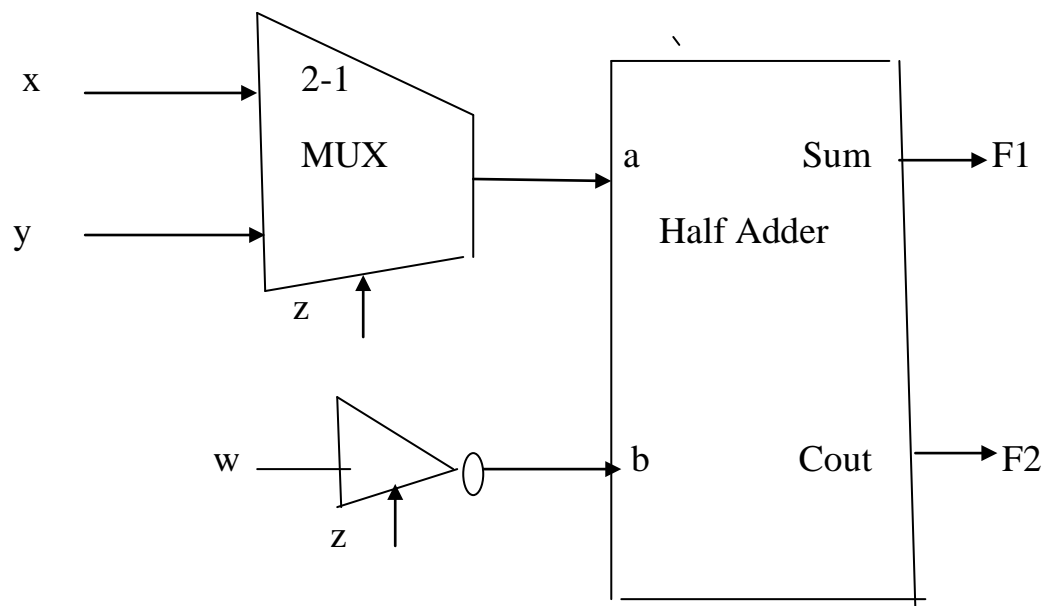Question [4]: (18 Marks)

Write the equations of the inputs a and b of the given Half Adder, then give the equations of $F1$ and $F2$.

Question [5]: (24 Marks)

  - a. Complete the timing diagram for the given Flip-Flop. (Assume the initial state of the F-F is equal to zero).



- b. Convert a J-K to S-R Flip-Flop showing all steps.